

# CprE 3810: Computer Organization and Assembly Level Programming

Processor Design

Henry Duwe  
Electrical and Computer Engineering  
Iowa State University

# Processor Design Approach


- Break operation down to steps even logic gates can understand
- Generally decompose into two kinds of operations:
  - Things that deal with the real data (datapath)
  - Things that control the stuff operating on the real data (control)
- Find a decomposition that is simple and efficient
- We will start simple
  - Later (in lecture and lab), we'll add features to improve performance

# The Processor: Datapath & Control

- Textbook RISC-V implementation simplified to contain only (added in slides):
  - Memory-reference instructions: **lw, sw**
  - Arithmetic-logical instructions: **add, sub, and, or, xor, slt, sltu**
  - Arithmetic-logical immediate instructions: **addi, andi, ori, xori, slti, sltiu**
  - Control flow instructions: **beq, j**
- Your lab version will require more instructions and thus modifications to this base design!
- Generic implementation:
  - Use the program counter (**PC**) to supply the instruction address and **fetch** the instruction from memory (and update the PC)
  - **Decode** the instruction (and read registers)
  - **Execute** the instruction (already built in lab)
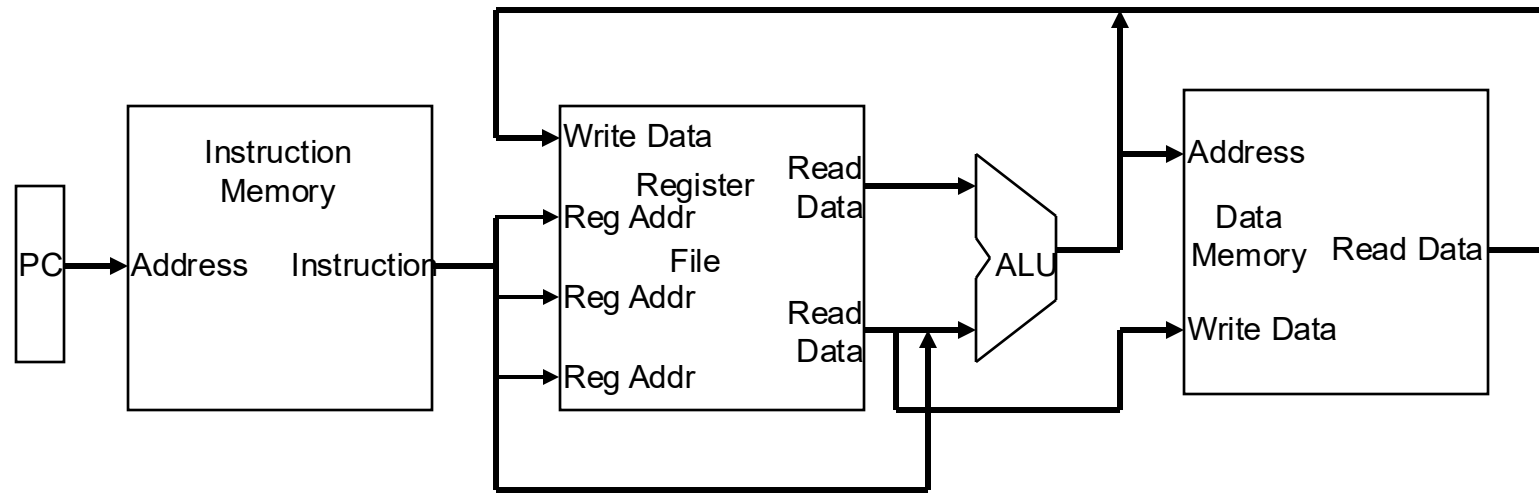
# Abstract Implementation View


- Two types of blocks:
  - Elements that operate on data values (combinational)
  - Elements that contain state (sequential)



- **Single cycle** operation
- Split memory (**Harvard**) model - one memory for instructions and one for data
 
# Edge-triggered Implementation



- An edge-triggered methodology, typical execution
  - Read contents of some state elements (combinational activity, so no clock control signal needed)
  - Send values through some combinational logic
  - Write results to one or more state elements on clock edge



- Assumes state elements are written on every clock cycle; if not, need explicit write control signal
  - Write occurs only when **both** the write control is asserted and the clock edge occurs
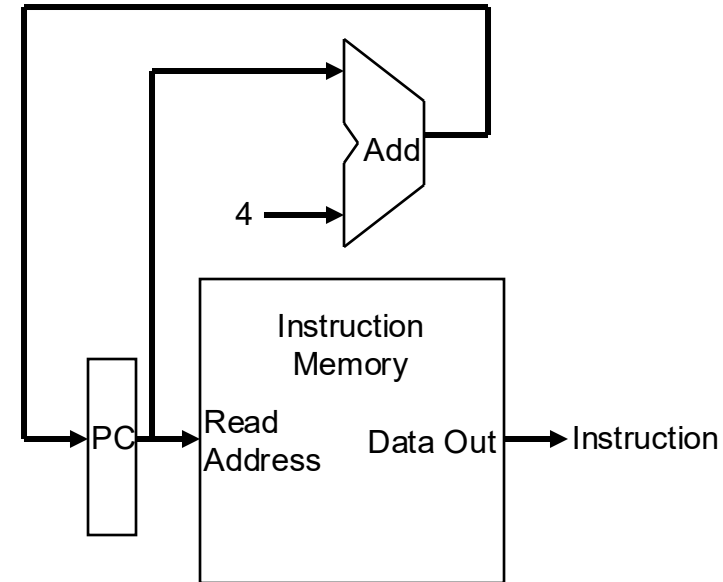 
# Fetching Instructions


- Fetching instructions involves
  - reading the instruction from the Instruction Memory
  - updating the PC value to be the address of the next (sequential) instruction



- PC is updated every clock cycle, so it does not need an explicit write control signal – just a clock signal
- Reading from the Instruction Memory is a combinational activity
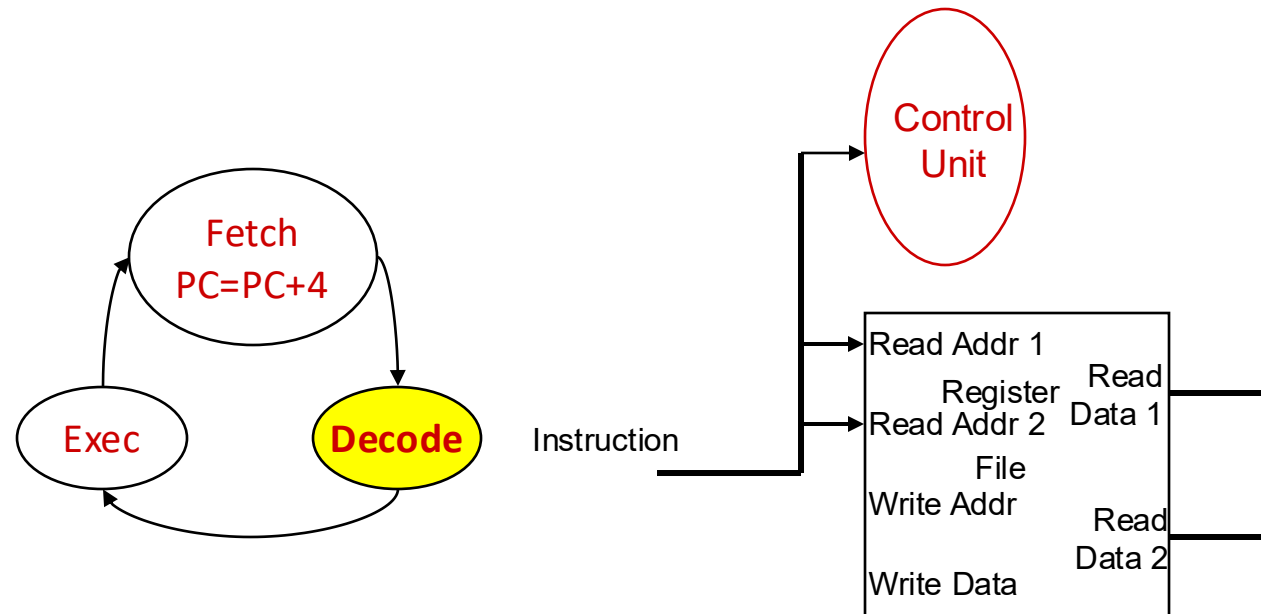
# Decoding Instructions

- Decoding instructions involves
  - Sending the fetched instruction's **opcode** and **function** field bits to the control unit



- Reading two values from the Register File
  - Register File addresses are contained in the instruction

# Reading Registers “Just in Case”

- Note that both RegFile read ports are active for **all** instructions during the Decode cycle using the `rs1` and `rs2` instruction field addresses
  - Since we haven’t decoded the instruction yet, we don’t know what the instruction is!
  - *Just in case* the instruction uses values from the RegFile do “work ahead” by reading the two source operands

Which instructions *do* make use of the RegFile values?



# Reading Registers “Just in Case”

- Note that both RegFile read ports are active for **all** instructions during the Decode cycle using the `rs1` and `rs2` instruction field addresses
  - Since we haven’t decoded the instruction yet, we don’t know what the instruction is!
  - *Just in case* the instruction uses values from the RegFile do “work ahead” by reading the two source operands


Which instructions *do* make use of the RegFile values?

- Also, all instructions (except **jal**) use the ALU **after** reading the registers


For what purpose? arithmetic? memory? control flow?
 
# Executing R Format Operations

- R format operations (**add**, **sub**, **slt**, **and**, **or**)



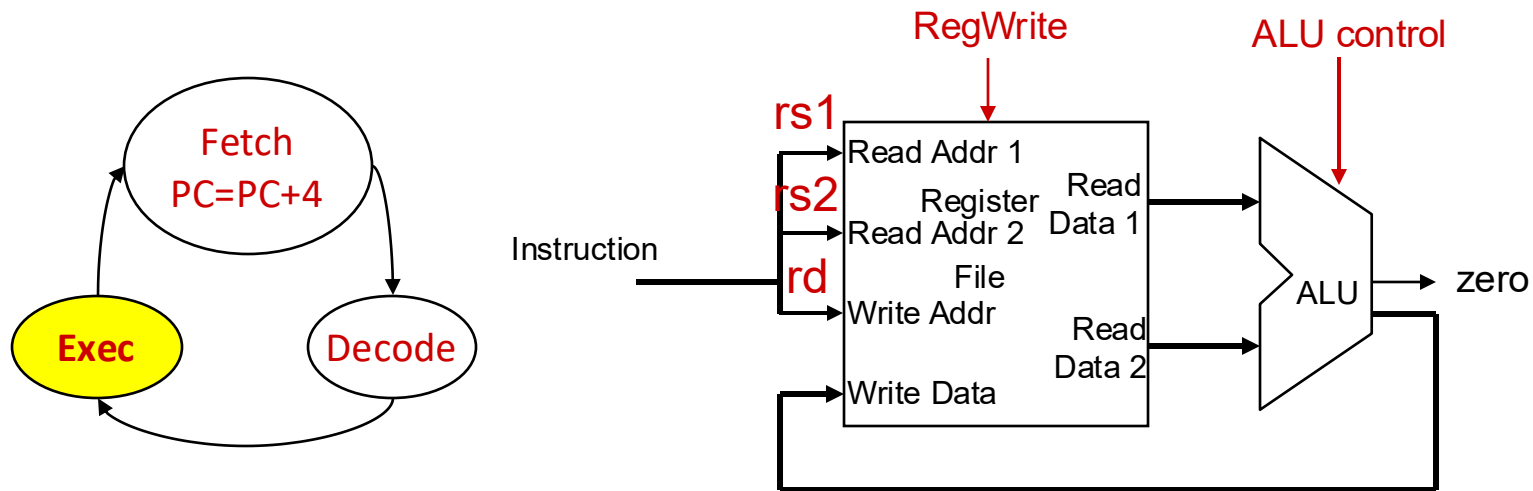- Perform operation (**op** and **funct**) on values in **rs1** and **rs2**
- Store the result back into the Register File (into location **rd**)




- Note that Register File is not written every cycle (e.g., **sw** or **beq**), so we need an explicit write control signal for the Register File

# Consider the `slt` Instruction

- Remember the R format instruction `slt`


```
slt t0, s0, s1    # if s0 < s1  
                  # then t0 = 1  
                  # else t0 = 0
```

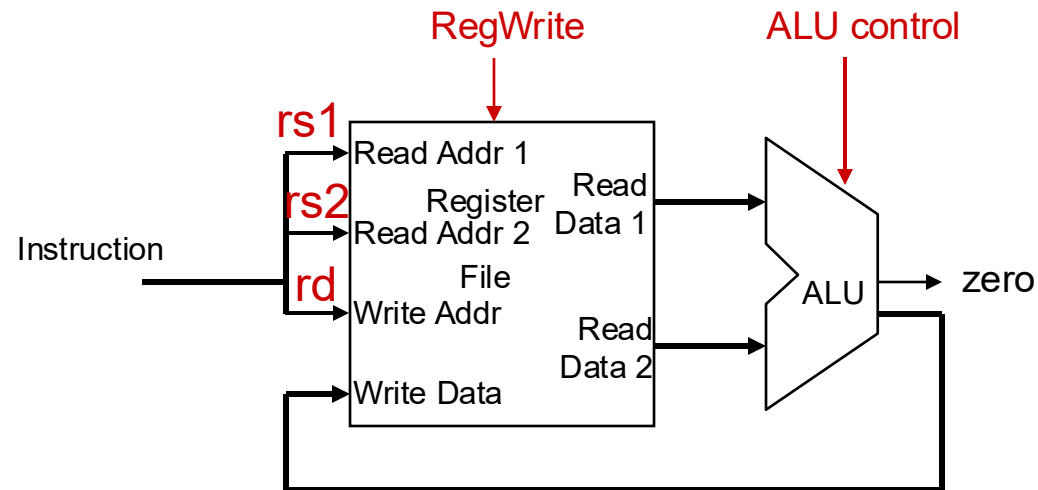- Where does the 1 (or 0) come from to store into t0 in the Register File at the end of the execute cycle?



# Executing Load Operations


- Load operations have to:

 

- Compute a memory address by adding the base register (in **rs1**) to the 12-bit signed offset field in the instruction
  - Base register was read from the Register File during decode
  - Offset value in upper 12 bits of the instruction must be sign extended to create a 32-bit signed value
- **Load** value, read from the Data Memory, must be stored in the Register File


# Executing Load and Store Operations

- Load and store operations have to:

 


- Compute a memory address by adding the base register (in **rs1**) to the 12-bit signed offset field in the instruction
  - Base register was read from the Register File during decode
  - Offset value in the upper 7 bits concatenated with bits 12:7 of the instruction must be sign extended to create a 32-bit signed value
- **Store** value, read from the Register File during decode (in **rs2**), must be written to the Data Memory

# Executing Load Operations (cont.)

 


# Executing Store Operations (cont.)

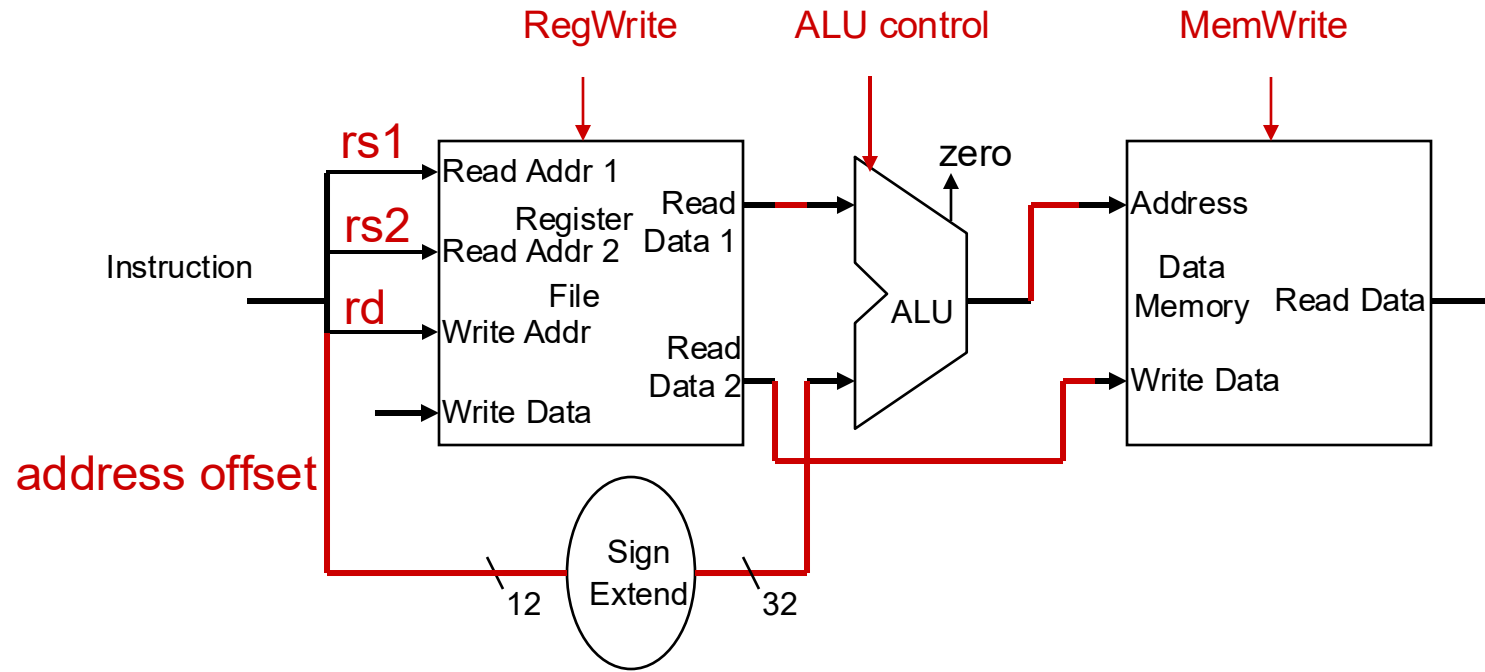

# Executing Branch Operations


- Branch operations have to

 

- Compare the operands read from the Register File during decode (**rs1** and **rs2** values) for equality (**zero** ALU output)
- Compute the branch target address by adding the PC to the 12-bit signed immediate field in the instruction that is concatenated with 1 bit of zero and sign extended
  - The “base register” is the PC
  - Offset value must be appropriately selected from the instruction and sign extended to create a 32-bit signed value and then shifted left 1 bits




# Executing Branch Operations (cont.)

 

 
# Executing Jump Operations

- Jump (**j****a****l** really) operations have to



- Compare the operands read from the Register File during decode (**rs1** and **rs2** values) for equality (**zero** ALU output)
- Compute the branch target address by adding the PC to the 12-bit signed immediate field in the instruction that is concatenated with 1 bit of zero and sign extended
  - The “base register” is the PC
  - Offset value must be appropriately selected from the instruction and sign extended to create a 32-bit signed value and then shifted left 1 bits

# Executing Jump Operations (cont.)

 

# Acknowledgments

- These slides contain material developed and copyright by:
  - Joe Zambreno (Iowa State)
  - David Patterson (UC Berkeley)
  - Mary Jane Irwin (Penn State)
  - Christos Kozyrakis (Stanford)
  - Onur Mutlu (Carnegie Mellon)
  - Krste Asanović (UC Berkeley)